

Chapter 2 Exercises: Combinational Logic and Boolean Algebra

Kyle Swanson

February 27, 2015

2.2 Write a Boolean equation in sum-of-products canonical form for each of the truth tables in Figure 2.81.

To determine this, look where $Y = 1$. Then just put complemented or not A, B, C, or D AND'ED together (Ex: If $B = 0$, complement it.). That is, turn the inputs to 1. And OR the results.

(a) $\overline{A}B = 1$, $A\overline{B} = 1$, $AB = 1$. Therefore
 $Y = \overline{A}B + A\overline{B} + AB$

(b) $Y = \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$

(c) $Y = \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$

(d) $Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}BCD + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$

(e) $Y = \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD$

2.4 Write a Boolean equation in product-of-sums canonical form for the truth tables in 2.81.

To determine this, look where $Y = 0$. Then just put complemented or not A, B, C, or D OR'ED together (Ex: If $B = 0$, do not complement it.). That is, turn the inputs to 0. And AND the results.

(a) $Y = (A + B)$

(b) $Y = (A + B + C)(\overline{A} + B + \overline{C})(\overline{A} + \overline{B} + \overline{C})$

(c) $Y = (A + B + C)(A + \overline{B} + C)(A + \overline{B} + \overline{C})(\overline{A} + B + C)(\overline{A} + B + \overline{C})$

(d) $Y = (A + B + C + \overline{D})(A + \overline{B} + C + D)(A + \overline{B} + C + \overline{D})(\overline{A} + B + C + \overline{D})(\overline{A} + B + \overline{C} + \overline{D})(\overline{A} + \overline{B} + C + D)(\overline{A} + \overline{B} + C + \overline{D})(\overline{A} + \overline{B} + \overline{C} + D)(\overline{A} + \overline{B} + \overline{C} + \overline{D})$

(e) $Y = (A + B + C + D)(A + B + C + \overline{D})(A + B + \overline{C} + D)(A + \overline{B} + C + D)(A + \overline{B} + C + \overline{D})(\overline{A} + \overline{B} + C + D)(\overline{A} + \overline{B} + C + \overline{D})(\overline{A} + \overline{B} + \overline{C} + D)(\overline{A} + \overline{B} + \overline{C} + \overline{D})$

2.6 Minimize each of the Boolean equations from Exercise 2.2.

(a) $Y = \overline{A}B + A\overline{B} + AB$
 $= \overline{A}B + A(\overline{B} + B)$ T5'
 $= \overline{A}B + A$

Finally, you can remove the \overline{A} . Due to T1 or T2. See the examples below for justification.

$$= A + B$$

Examples on why \overline{A} can be eliminated.

$$A = 1, B = 1. \quad 0 \text{ and } 1 \text{ or } 1 = 1 \Leftrightarrow 1 \text{ or } 1 = 1$$

$$A = 0, B = 1. \quad 1 \text{ and } 1 \text{ or } 0 = 1 \Leftrightarrow 1 \text{ or } 0 = 1$$

$$A = 1, B = 0. \quad 0 \text{ and } 0 \text{ or } 1 = 1 \Leftrightarrow 0 \text{ or } 1 = 1$$

$$A = 0, B = 0. \quad 1 \text{ and } 0 \text{ or } 0 = 0 \Leftrightarrow 0 \text{ or } 0 = 0$$

See how they're the same? Since \overline{A} and B are AND'ed together, \overline{A} doesn't matter since it has A on the other side of an OR.

$$\begin{aligned} \text{(b)} \quad Y &= \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C \\ &= \overline{A}(\overline{B}C + B\overline{C} + BC) + \overline{C}(A\overline{B} + AB) \quad \text{T8} \\ &= \overline{A}(C(\overline{B} + B) + B\overline{C}) + A\overline{C} \quad \text{T5, T3} \\ &= \overline{A}(B\overline{C} + C) + A\overline{C} \\ &= \overline{A}(B + C) + A\overline{C} \\ &= \overline{A}B + \overline{A}C + A\overline{C} \end{aligned}$$

$$\text{(c)} \quad Y = \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$$

$$\text{(d)} \quad Y = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D}$$

$$\text{(e)} \quad Y = \overline{A}\overline{B}CD + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D} + A\overline{B}CD$$

2.8 Sketch a reasonably simple combinational circuit implementing each of the functions from Exercise 2.6.

2.14 Simplify the following Boolean equations using Boolean theorems. Check for correctness using a truth table or K-map.

$$\text{(a)} \quad Y = \overline{A}BC + \overline{A}B\overline{C}$$

$$\text{(b)} \quad Y = \overline{A}\overline{B}\overline{C} + A\overline{B}$$

$$\text{(c)} \quad Y = ABC\overline{D} + \overline{A}BC\overline{D} + (\overline{A + B + C + D})$$

2.16 Sketch a reasonably simple combinational circuit implementing each of the functions from Exercise 2.14.

2.22 Prove that the following theorems are true using perfect induction. You need not prove their duals.

- (a) The idempotency theorem (T3)
- (b) The distributivity theorem (T8)
- (c) The combining theorem (T10)